

**EXPERIMENT NO:-7**

➤ **AIM:** To design and test 1-bit Magnitude comparator.



➤ **APPARATUS:** Breadboard, jumpers wires, IC's, LED's, power supply.

➤ **THEORY:**

The 1 bit magnitude comparator is a combinational circuit that compares magnitude of two 4 bit numbers to make either of its O/P ( $A > B$ ,  $A = B$ ,  $A < B$ ) at logic high level.

Let  $A = A_0$  &  $B = B_0$  are 1-bit number respectively. The 1-bit magnitude comparator compares magnitudes as per following expressions for outputs.

Let  $x_i$  will be at logic high level when  $A_i$  &  $B_i$  are at equal level. ( $i = 0, 1$ )

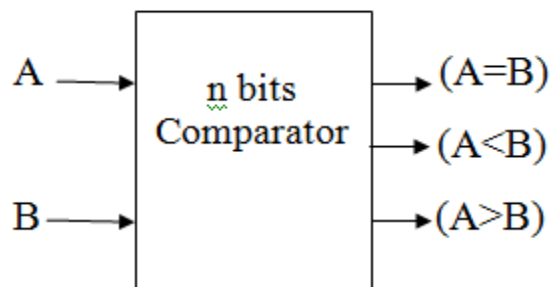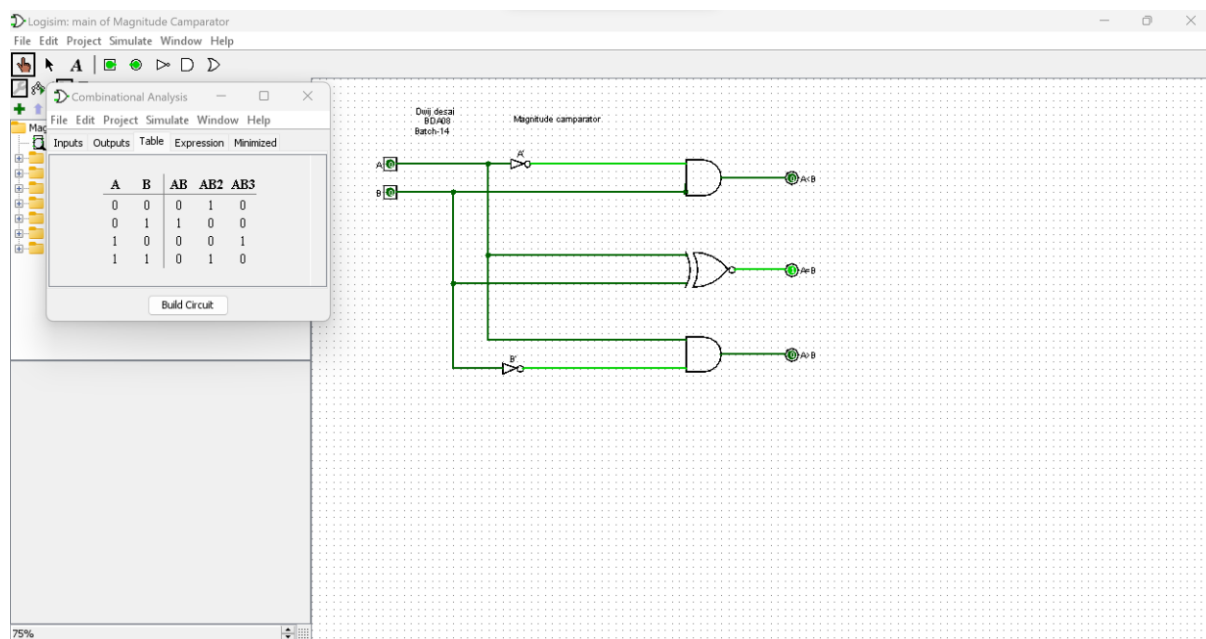***BLOCK DIAGRAM OF 1-BIT MAGNITUDE COMPARATOR:******CIRCUIT DIAGRAM OF 1-BIT MAGNITUDE COMPARATOR:******TRUTH TABLE***

A	B	$A < B$	$A = B$	$A > B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0