


**EXPERIMENT NO:-8**


➤ **AIM:** To design and test multiplexer / de-multiplexer circuit.

➤ **APPARATUS :** Logisim simulator.

➤ **THEORY:**

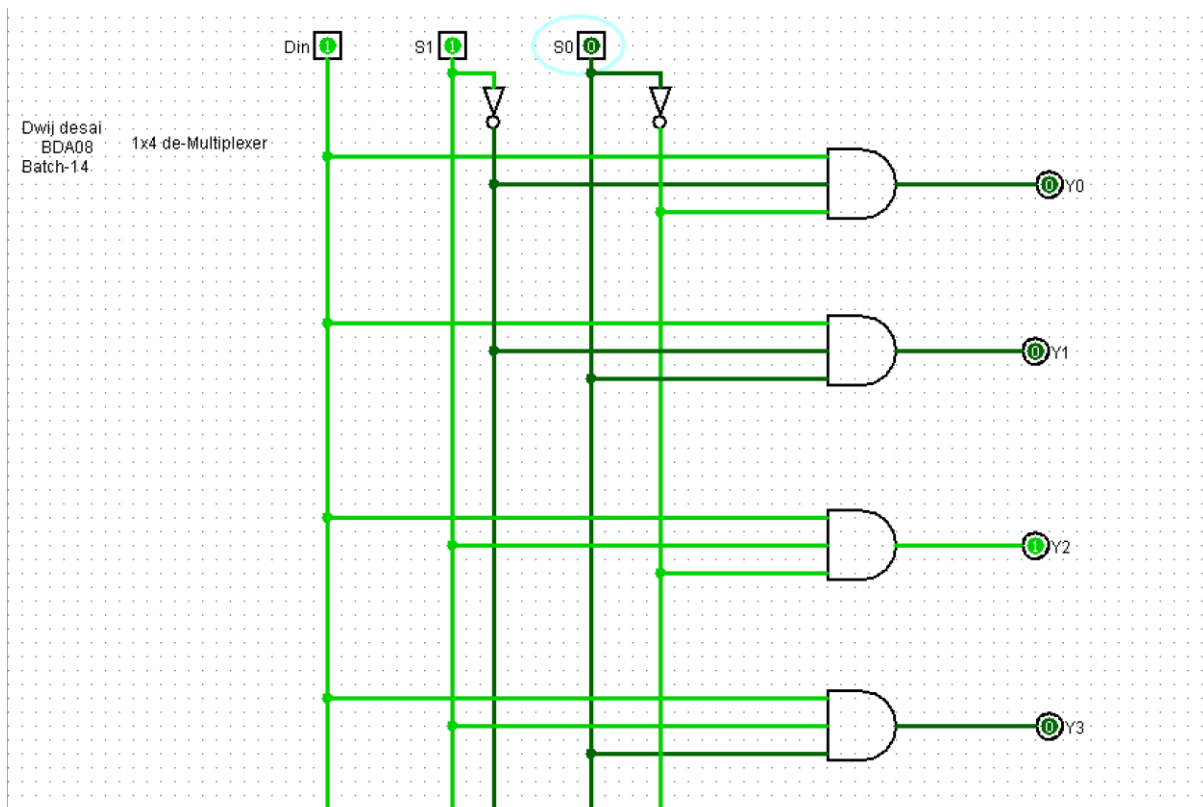(It includes circuit description, truth table, circuit diagram and logical explanation.)



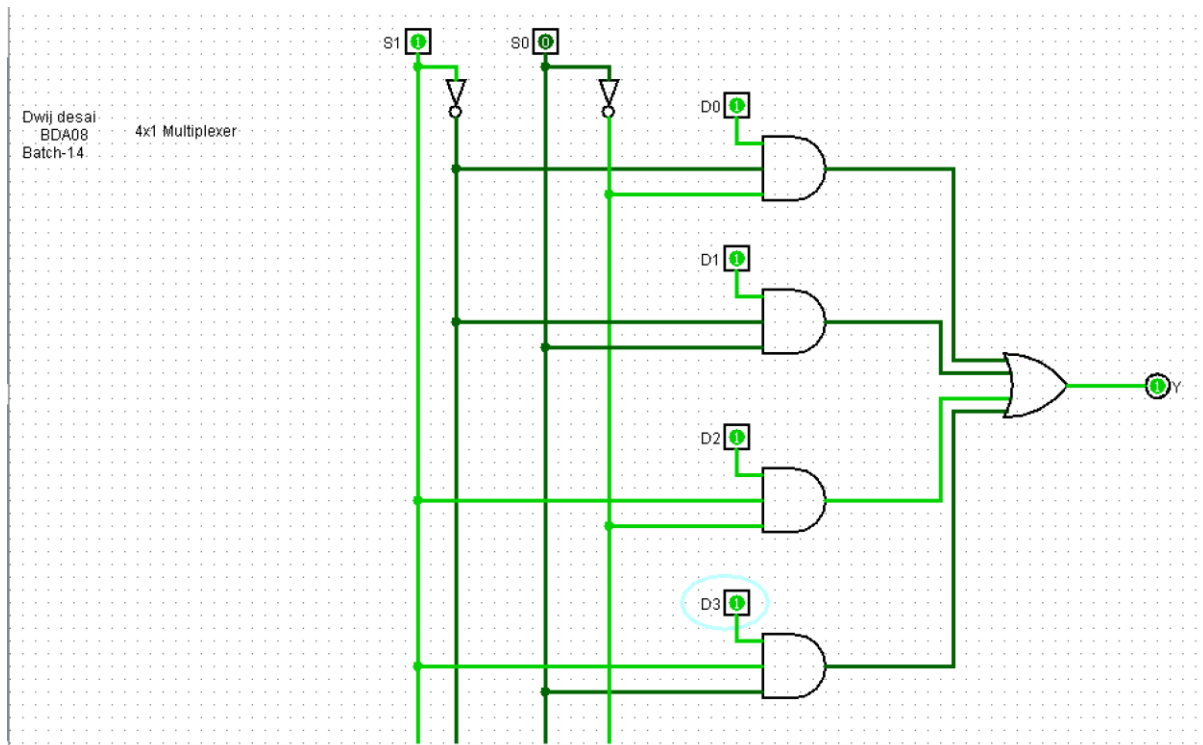**➤ PROCEDURE:**

- Design the circuit using Truth Table and K-Map.
- Use Logisim simulator
- Take appropriate components/gates from part selection
- Place it on mains, define the respective values
- connect appropriate with inputs and output bits with the components/gates.
- Run the simulator and observe the results.
- Test the truth table of each converter circuit.

**➤ CONCLUSION:**

- Multiplexer takes 4 input and gives and gives 1 output so it's name 4x1 Multiplexer.
- De-multiplexer takes 1 input and give 4 output hence the name 1x4 De-multiplexer, it helps user to control the output of certain component.

**➤ Exercise:**

Implement an 8x1 Mux by using 4x1 Mux

