

**EXPERIMENT NO:-6**

➤ **AIM:** To **Design and test decoder circuit.**

➤ **APPARATUS:** Logisim simulator


➤ **THEORY:**

Discrete quantities of information are represented in digital systems with binary codes. A binary code of  $n$  bits is capable of representing up to  $2^n$  distinct elements of the coded information. A decoder is a combinational circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines. If the  $n$ -bit decoded information has unused or don't-care combinations, the decoder output will have less than  $2^n$  outputs.

The decoders presented here are called  $n$ -to- $m$  line decoders where  $m \leq 2^n$ . Their purpose is to generate the  $2^n$  (or less) minterms of  $n$  input variables. The name decoder is also used in conjunction with some code such as BCD-to-seven-segment decoder.

Consider the 3 to 8 line decoder circuit. The three inputs are decoded into eight outputs. Each output representing one of the minterms of the 3-input variables. The three inverters provide the complement of the outputs, and each one of eight AND gates generate one of the minterms. A particular application of this decoder would be a binary to octal conversion. The input variables may represent a binary number, and the outputs will then represent the eight digits in the octal number system. However a 3-to-8-line decoder can be used for decoding and 3-bit code to provide eight outputs, one for each element of the code.

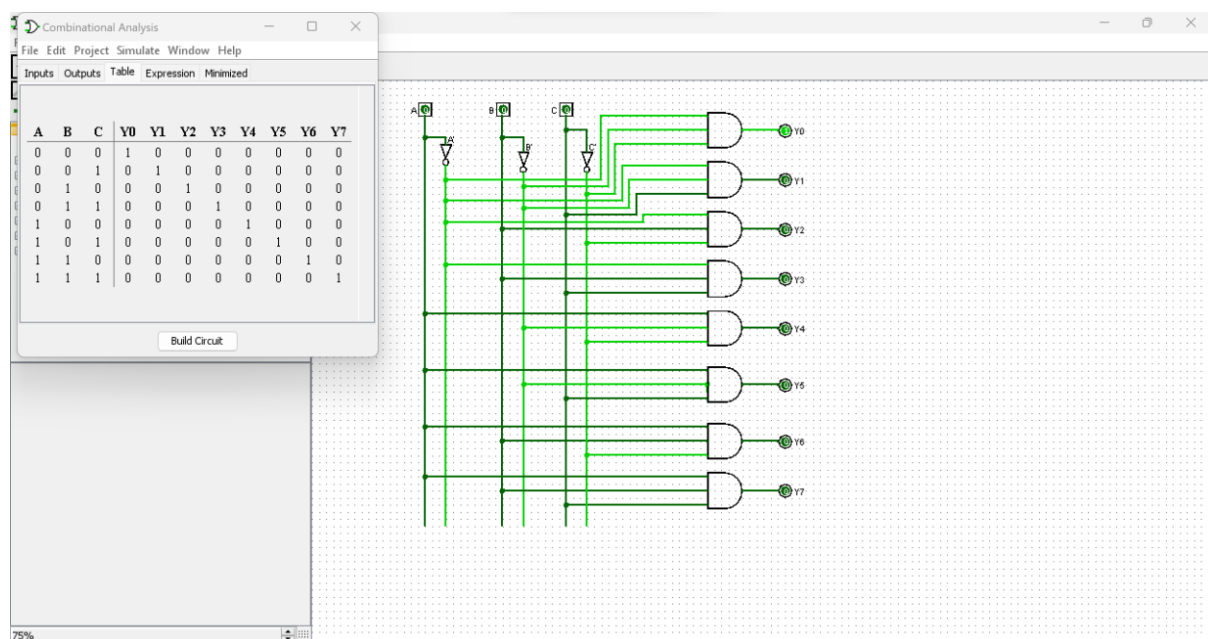**CIRCUIT DIAGRAM OF 3 TO 8 BIT DECODER:**



**TRUTH TABLE OF 3 TO 8 BIT DECODER:**

INPUTS				OUTPUTS							
ENABLE	ADDRESS LINES										
EN	A	B	C	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	0	0
1	1	1	0	0	0	0	0	0	0	1	0
1	1	1	1	0	0	0	0	0	0	0	1

**CONCLUSION** - Designing and testing a decoder circuit (using AND - NOT) is a fundamental exercise in digital electronics, providing practical experience and reinforcing key concepts in binary decoding and logic circuits.